


Answer on Question #52417 - Engineering, Other

Question

A single-phase circuit consists of three parallel branches, the currents in which are, respectively, in amperes: $i_1 = 20 \sin(314t)$, $i_2 = 30 \sin(314t - \pi/4)$, and $i_3 = 18 \sin(314t + \pi/2)$. The supply voltage is $u = 200 \sin(314t)$ volts.

- What is the frequency of the current?
- Using the graph paper and a scale of 1 cm per 5 A, plot a phasor diagram and determine the overall current taken from the supply (r.m.s. value) and its phase angle.
- Determine the active and reactive currents.
- Express the total current in the trigonometric form similar to that for the branch currents.
- Find the impedance, resistance and reactance of the circuit.
- Find the conductance, admittance and susceptance of the circuit.

Solution

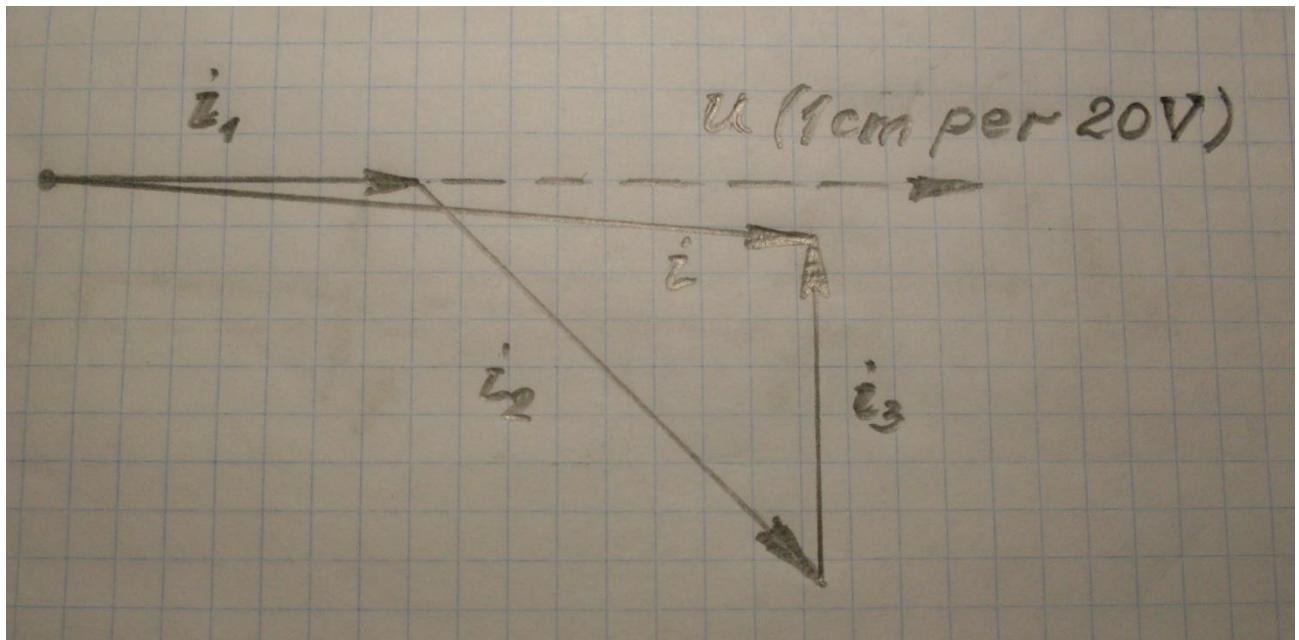


- in general we have for harmonic oscillations:

$$i = i_{max} \times \sin(\omega t + \varphi_0) \text{ or } u = u_{max} \times \sin(\omega t + \varphi_0),$$

comparing the general view of the data provided notice $\omega = 314 \text{ rad/s}$ – cyclic frequency,
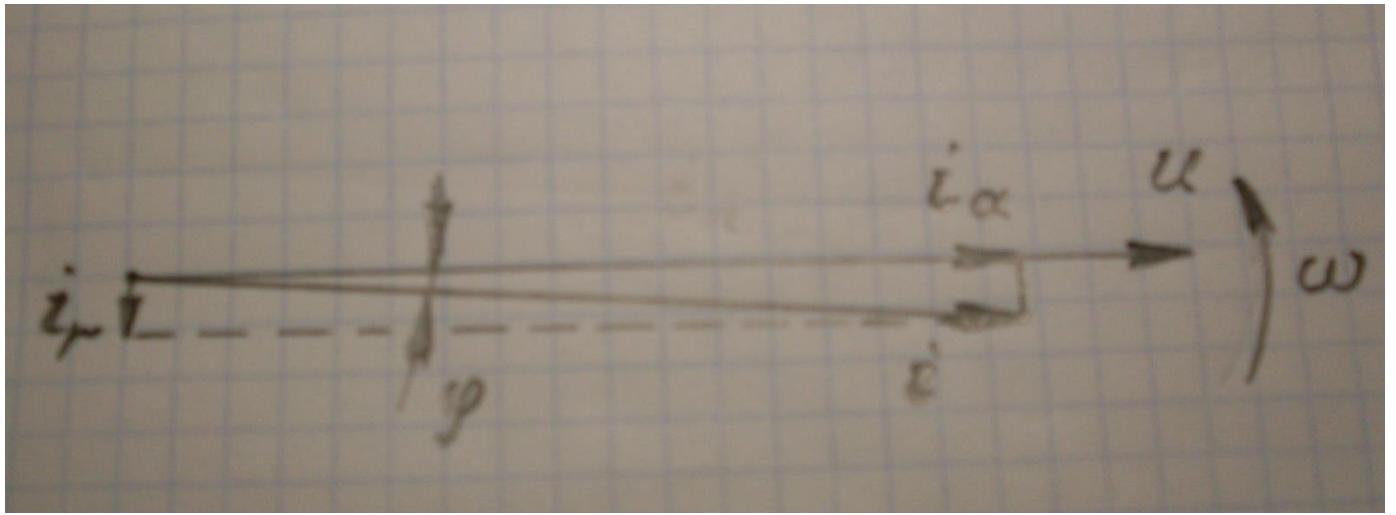
$$\text{because } \omega = 2\pi v, \text{ therefore frequency } v = \frac{\omega}{2\pi} = \frac{314}{2 \times 3.14} = 50(\text{Hz});$$



b,c) the currents and phase angle:

the length of the segment corresponding to the total current is 8.4 cm,
therefore, the approximate value of the total current is $i = 8,4 \times 5 = 42 (A)$,

similarly, the active current $i_a = 8,39 \times 5 = 41,9 (A)$, reactive current $i_r = 0,6 \times 5 = 3 (A)$,

$$\text{phase angle } \varphi = \arctg \frac{i_r}{i_a} = \arctg \frac{3}{41,9} = 0,071 \text{ (rad)};$$

d) the total current in the trigonometric will look like:

$$i = 42 \sin(314 t - 0,071), A;$$

e) the impedance, resistance and reactance of the circuit are:

?

f) the conductance, admittance and susceptance of the circuit are:

?

Answer: 50 Hz, 42A, 0.071 rad, 41.9 A, 3 A, $i = 42 \sin(314 t - 0,071)$, ...