

### **Answer on Question #55428-Engineering-Electrical Engineering**

An \_\_\_\_\_ amplifier can perform operations, such as addition, subtraction, differentiation or integration efficient

operational

optimizing

consistent

### **Answer**

#### **Operational.**

*Operational amplifiers* can be used to perform mathematical operations on voltage signals such as inversion, addition, subtraction, integration, differentiation, and multiplication by a constant.