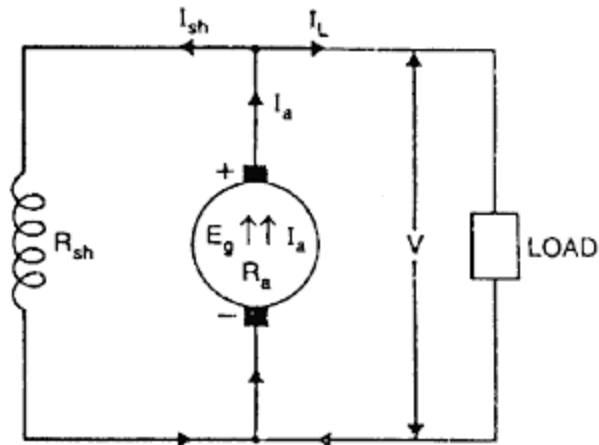


## Answer on Question #64392, Engineering / Electrical Engineering

A 100-kW, 250-V DC shunt generator has an armature resistance of  $0.05\Omega$  and a field circuit resistance of  $60\Omega$ . With the generator operating at rated voltage, determine the induced voltage at full load.

### Solution:

In a shunt generator, the field winding is connected in parallel with the armature winding so that terminal voltage of the generator is applied across it.



At full load, the terminal voltage

$$V = E_g - I_a R_a$$

Shunt field current,

$$I_{sh} = \frac{V}{R_{sh}} = \frac{250\text{ V}}{60\ \Omega} = 4.17\text{ A}$$

Load current,

$$I_L = \frac{P}{V} = \frac{100,000\text{ W}}{250\text{ V}} = 400\text{ A}$$

Armature current,

$$I_a = I_L + I_{sh} = 400 + 4.17 = 404.17\text{ A}$$

Induced voltage,

$$E_g = V + I_a R_a = 250\text{ V} + (404.17\text{ A}) \times (0.05\ \Omega) = 270.2\text{ V}$$

**Answer:** 270.2 V