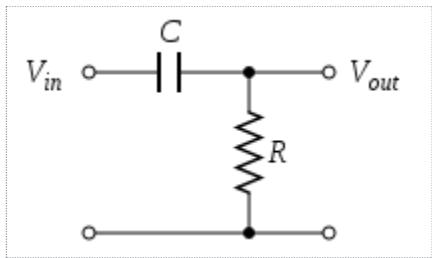


Answer on question #85268, Engineering Electrical Engineering

Design and draw π - type high pass filter having cut off frequency of 2kHz and load resistance of 500Ω .

Solution



$$C = \frac{1}{2 \cdot \pi \cdot f \cdot R} = \frac{1}{2 \cdot 3.14 \cdot 2000 \cdot 500} = 0.1592 \cdot 10^{-6} F$$

$$R = 500 \text{ Ohm}$$

$$f = 2000 \text{ Hz}$$

Answer provided by www.AssignmentExpert.com