

## **ANSWER on Question #72344 – Math – Calculus**

### **QUESTION**

Here is the information about the circuit :

$$\text{Capacitor} = 100 \text{ nF} \rightarrow C = 100 \cdot 10^{-9} \text{ F} \equiv 10^{-7} \text{ F} \rightarrow C = 10^{-7} \text{ F}$$

$$\text{Resistor} = 47 \text{ k}\Omega \rightarrow R = 47 \cdot 10^3 \Omega$$

$$\text{Supply voltage} = 5 \text{ V} \rightarrow V_0 = 5 \text{ V}$$

Investigate the meaning of ‘time constant’ and from your graph estimate a value. Compare this with your calculated one.

### **SOLUTION**

**Charging characteristic for a series capacitive circuit is**

$$V(t) = V_0 \left( 1 - e^{-\frac{t}{T}} \right), \text{ where}$$

$$T = RC - \text{is called the time constant.}$$

In our case,

$$T = 47 \cdot 10^3 \cdot 10^{-7} = 47 \cdot 10^{-4} = 4.7 \cdot 10^{-3} \equiv 4.7 \text{ (ms) (milliseconds)}$$

To find this given constant from the experimental data, we transform the initial formula.

$$\begin{aligned} V(t) = V_0 \left( 1 - e^{-\frac{t}{T}} \right) \rightarrow 1 - e^{-\frac{t}{T}} &= \frac{V(t)}{V_0} \rightarrow -e^{-\frac{t}{T}} = \frac{V(t)}{V_0} - 1 \rightarrow e^{-\frac{t}{T}} = 1 - \frac{V(t)}{V_0} \\ -\frac{t}{T} &= \ln \left( 1 - \frac{V(t)}{V_0} \right) \end{aligned}$$

Now we are plotting the graph: on the  $Ox$  axis, we set aside time (in milliseconds); on the  $Oy$  axis, we set off this value  $\ln \left( 1 - \frac{V(t)}{V_0} \right)$ .

In such coordinates, the graph will be a straight line, and in order to find a “time constant” we need evaluate :

$$T = \frac{-1}{\text{the slope of the straight line}}.$$

Answer provided by <https://www.AssignmentExpert.com>