

### Question

What is the thermal energy developed when a current of 1.5 A passed through a resistor of resistance of 10ohm for 10 seconds ?

### Solution

We are given:

$$I=1.5A$$

$$R=10 \text{ Ohm}$$

$$t=10 \text{ s}$$

According to the Joule-Lenz law:  $Q=I^2 \cdot R \cdot t$ .

where  $Q$  – thermal energy ( J),  $I$  - current (A),  $R$  – resistance (Ohm),  $t$ -time ( s).

Calculating:  $Q=I^2 \cdot R \cdot t = 1.5^2 \cdot 10 \cdot 10 = 22.5 \text{ J}$

Answer: 22.5 J