

1. A basic LED driver circuit is comprised of a 5 volt source a 2 kohm potentiometer and a LED. The LED is forward biased. The LED manufacturer indicates a maximum current rating of 20 mA at a diode voltage drop of 1.9 volts.

- a.) What is the minimum value of resistance the potentiometer can be adjusted to before damage to the LED occurs?
- b.) What is the nominal resistance of the LED with this condition?
- c.) Draw a schematic diagram illustrating the addition of a component that will protect the LED in the event that the pot is adjusted below a safe level.

Solution

1).

$$\frac{U}{I} = R + \frac{U_{diode}}{I}$$

$$\frac{5}{0.02} = R + \frac{1.9}{0.02}$$

$$R = 250 - 95 = 155 \text{ Ohm}$$

2).

$$R_{diode} = \frac{U_{diode}}{I} = \frac{1.9}{0.02} = 95 \text{ Ohm}$$

3).

