

Question#18474

Two resistors, having resistances of 30 and 60 ohms are connected in parallel, and in series with them is a resistor having a resistance of 5 ohms. What p.d. must be applied to the whole circuit to cause a current of 4.8 Amps through the 5 ohm resistor?

Solution:

Let:


$$R_1 = 30 \text{ ohm}$$

$$R_2 = 60 \text{ ohm}$$

$$R_3 = 5 \text{ ohm}$$

$$I = 4.8 \text{ Amp}$$

$$U = ?$$

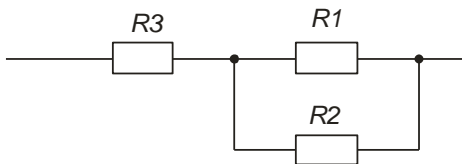

The current through the resistor R3 is equal to total current through circuit and according to the Ohm's Law is:

$$I = \frac{U}{R_z}, \text{ where } R_z \text{ the total resistance of the circuit}$$

$$R_z = R_3 + \frac{R_1 * R_2}{R_1 + R_2} = 5 + \frac{30 * 60}{30 + 60} = 25 \text{ ohm}$$

$$U = IR_z = 4.8 * 25 = 120 \text{ V}$$

Answer: 120 V