

Question#19746

12 volts is applied across a 4 ohm resistor. How much power is dissipated by the resistor?

Answer:

$W = IU$, Where I – current, voltage

According to the Ohm's law:

$$I = \frac{U}{R} \gg$$

$$W = \frac{U}{R}U = \frac{U^2}{R}$$

$$W = \frac{12^2}{4} = 36 \text{ W}$$

Answer: 36 W.