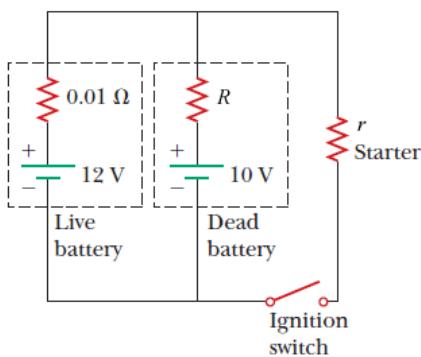


Task:

A dead battery is charged by connecting it to the live battery of another car with jumper cables (see figure). (Take $R = 2.03 \Omega$ and $r = 0.09 \Omega$. For this problem, if your answers are used in any subsequent calculations, make sure to base your calculation on the rounded values)

(a) Determine the current in the starter.

(b) Determine the current in the dead battery.

Solution:

I'll list all resistors in milliohms for ease of calculation.

Use superposition.

1. Replace **10 V battery** with a short. Parallel combo of $2030 \text{ m}\Omega$ and $90 \text{ m}\Omega$ is $86.18 \text{ m}\Omega$. That is in series with $10 \text{ m}\Omega$ for total of $96.18 \text{ m}\Omega$. **Total Current** is $12 \text{ V} / 96.18 \text{ m}\Omega = 124.77 \text{ A}$. That produces a voltage across the starter of 10.75 V , and a current through it of 119.47 A .

2. Replace **12 V battery** with a short. Parallel combo of $10 \text{ m}\Omega$ and $90 \text{ m}\Omega$ is $9 \text{ m}\Omega$. That is in series with $2030 \text{ m}\Omega$ for total of $2039 \text{ m}\Omega$. Total Current is $10 \text{ V} / 2039 \text{ m}\Omega = 4.904 \text{ A}$. That produces a voltage across the starter of 0.044 V , and a current through it of 0.49 A .

Total current is the sum, $119.47 \text{ A} + 0.49 \text{ A} = 119.96 \text{ A}$

this means the voltage across the starter of is 10.796 V .

The voltage across R is $10.796 \text{ V} - 10 \text{ V} = 0.796 \text{ V}$

The current through R is $0.796 \text{ V} / 2030 \text{ m}\Omega = 0.392 \text{ A}$, downwards

Answer:

(a) Total current is 119.96 A

(b) The current through R is 0.392 A , downwards