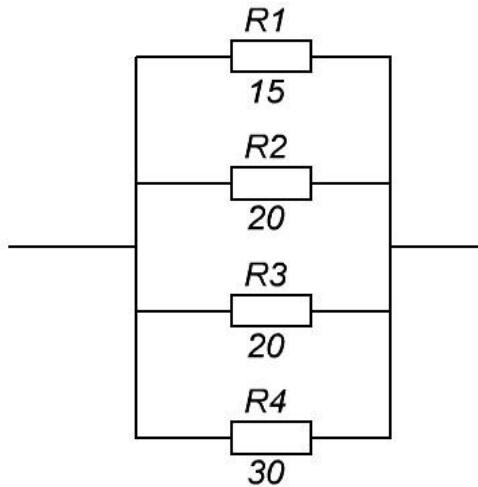


It's known that smallest resistance we can reach when using parallel connection, as on the circuit below.



Using parallel connection rule:


$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$\frac{1}{R} = \frac{1}{15} + \frac{1}{20} + \frac{1}{20} + \frac{1}{30} = \frac{4 + 6 + 2}{60} = \frac{12}{60} = \frac{1}{5} \left(\frac{1}{\Omega}\right)$$

So,

$$R = 5 \Omega$$

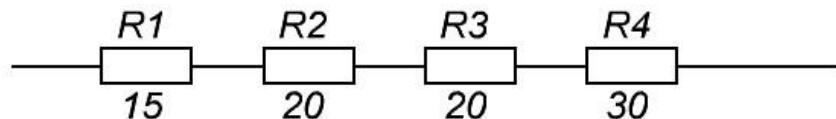It's known that smallest resistance we can reach when using series connection, as on the circuit below.



Using series connection rule:

$$R = R_1 + R_2 + R_3 + R_4$$

$$R = 15 + 20 + 20 + 30 = 85 \Omega$$