

You are given a number of 10 ohm resistors capable of dissipating only 1.0 W without being destroyed. What is the minimum number of such resistors that you need to combine in series or parallel combinations to a 10 ohm resistor that is capable of dissipating at least 5.0 W? Draw the circuit diagram showing the arrangement you propose to achieve the above result?

**Solution:**

$P=R \cdot I^2$ , where  $P$  is power,  $R$  is resistance,  $I$  is current

$$I^2 = P/R$$

$$I^2 = 5/10 = 0.5$$

$$I = 0.7 \text{ amp}$$

4 Resistors are combined in parallel.

Sum resistance is  $R_s = 2.5 \text{ ohm}$

We need to combine it to 10 ohm. It's 4 "blocks".

$U=I \cdot R$  where  $U$  is voltage on resistor

$$U = 1.75$$

$$P = (U^2)/R$$

$P = 0.3 \text{ W}$  it's power on one resistor.

**Answer:**

