

Question 36857

The power, dissipated by resistor is $P=IU$, or using Ohms law $I=\frac{U}{R}$,

$$P=\frac{U^2}{R}=\frac{(12V)^2}{4\Omega}=36\text{ W} .$$