

A current flows through a resistance  $R=10$  Ohm what is the expression for instantaneous voltage across the resistance when a)  $i=5\sin 314t$  b)  $i=10\sin(1570-45')$

**Solution.**

$$R = 10 \text{ Ohm};$$

a)  $i = 5\sin 314t;$

b)  $i = 10\sin(1570 - 45');$

a)  $u - ?$

b)  $u - ?$

A general expression for instantaneous current:

$$i = I_{max} \sin(\omega t + \varphi_0).$$

A general expression for instantaneous voltage across the resistance:

$$u = U_{max} \sin(\omega t + \varphi_0).$$

$I_{max}$  - the peak current;

$U_{max}$  - the peak voltage;

$\varphi_0$  – the phase shift.

By Ohm's law:

$$I_{max} = \frac{U_{max}}{R};$$

$$U_{max} = I_{max}R.$$

$$u = I_{max}R \sin(\omega t + \varphi_0).$$

a)  $i = 5\sin 314t;$

$$I_{max} = 5A.$$

The expression for instantaneous voltage across the resistance:

$$u = 5 \cdot 10 \sin 314t = 50 \sin 314t.$$

b)  $i = 10\sin(1570 - 45');$

$$I_{max} = 10A.$$

The expression for instantaneous voltage across the resistance:

$$u = 10 \cdot 10 \sin(1570 - 45') = 100 \sin(1570 - 45').$$

**Answer:** a) The expression for instantaneous voltage across the resistance is  $u = 50\sin 314t$ .  
b) The expression for instantaneous voltage across the resistance is  $u = 100\sin(1570 - 45')$ .