

Answer on Question #40550, Physics, Electric Circuits

A 10Ω and a 20Ω resistances are connected in parallel, another resistance of 5Ω is connected in series with the two. If the supply voltage is $48V$, what is the current through the 10Ω resistance?

Solution

Total resistance is

$$R = \frac{R_1 R_2}{R_1 + R_2} + R_3,$$

where $R_1 = 10\Omega$, $R_2 = 20\Omega$ and $R_3 = 5\Omega$. So

$$R = \frac{10 \cdot 20}{10 + 20} + 5 = 11.7\Omega.$$

Total current is

$$I = \frac{U}{R} = \frac{48V}{\frac{35}{3}\Omega} = 4.1A.$$

But the total current is equal the sum of currents through a 10Ω and a 20Ω resistances:

$$I = I_1 + I_2.$$

In consequence of parallel connection of 10Ω and a 20Ω resistances the voltages across them are equal each other:

$$I_1 R_1 = I_2 R_2.$$

Thus

$$I = I_1 + \frac{I_1 R_1}{R_2}.$$

The current through the 10Ω resistance:

$$I_1 = \frac{I}{1 + \frac{R_1}{R_2}} = \frac{4.1}{1 + \frac{10}{20}} = 2.7A.$$

Answer: 2.7A.