

Answer on Question #41185, Physics, Electric Circuits

Question: A step down transformer is connected to main supply 200V to

operate a 6V-30W bulb. The current in primary-

A) 3 Amp. B) 0.3 Amp. C) 1.5 Amp. D) 0.15 Amp.

Solution. The current is secondary is

$$I = \frac{P_2}{U_2} = \frac{30W}{6V} = 5 A$$

Now we can find current in primary.

$$U_1 I_1 = U_2 I_2$$

$$I_1 = \frac{U_2 I_2}{U_1} = \frac{6 \cdot 5}{200} = 0.15 A$$

The answer is D) 0.15 Amp.