

Answer on Question #43356, Physics, Other

Task:

In the common base circuit the emitter current $I_e=5\mu\text{A}$ and the collector current $I_c=50\mu\text{A}$ and the emitter circuit resistance $R_e=10\text{ ohm}$ collector $R_c=50\text{k ohm}$. Find power amplification factor

Solution:

Let power amplification factor= K_p ; input power P_{in} ; output power P_{out} ;

$$K_p = 10\lg \frac{P_{out}}{P_{in}} = 10\lg \frac{I_c^2 \cdot R_c}{I_e^2 \cdot R_e} = 10\lg \frac{(50 \cdot 10^{-6})^2 \cdot 50 \cdot 10^3}{(5 \cdot 10^{-6})^2 \cdot 10} = 10\lg 5 \cdot 10^5 \approx 56.98\text{dB}$$

Answer: $K_p=56.98\text{Db}$