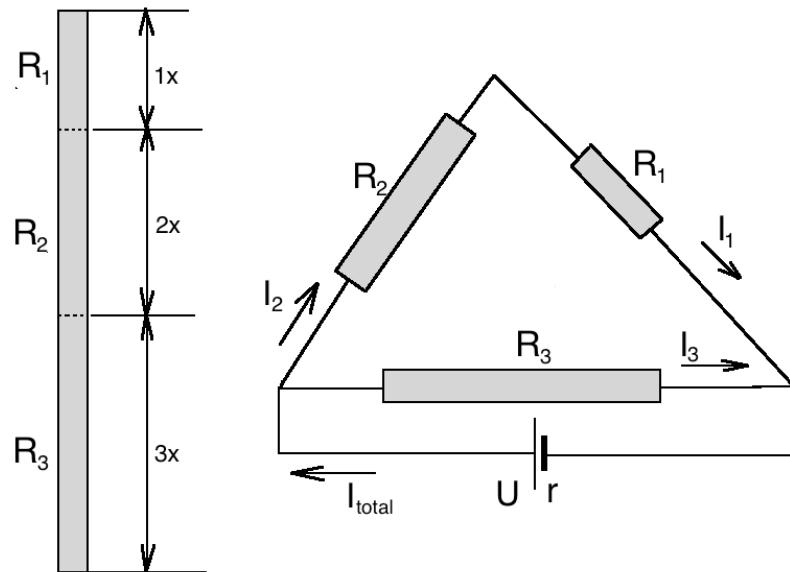


Answer on Question #43573 – Physics - Electric Circuits

a uniform wire of resistance 15 ohms is cut into three pieces in ratio 1:2:3 and the three pieces are connected to form a triangle. a cell of 10V potential with internal resistance 1 ohm is connected across the highest of three resistors. calculate the current through each part of the circuit.

Solution:



$R = 15 \text{ Ohm}$ – resistance of the uniform wire;

$1x : 2x : 3x$ – ratio of the three pieces;

$U = 10V$ – potential of the cell;

$r = 1 \text{ Ohm}$ – internal resistance of the cell;

Since the resistance is linearly proportional to the length of the wire ($R = \rho \frac{L}{S}$, L – length), the ratio of the three resistances of the pieces is equal to the ratio of the lengths of the pieces:

$$R_1 : R_2 : R_3 = 1 : 2 : 3$$

$$R_3 = 3R_1$$

$$R_2 = 2R_1$$

The sum of these resistances is equal to the resistance of the uniform wire. We have an equation:

$$R = R_1 + R_2 + R_3$$

$$R = R_1 + 2R_1 + 3R_1$$

$$R = 6R_1$$

$$R_1 = \frac{R}{6}; R_2 = \frac{2R}{6}; R_3 = \frac{3R}{6} = \frac{R}{2}$$

In a series configuration, the current through all of the resistors is the same, and resultant resistance is equal to the sum of the resistances:

$$R_{12} = R_1 + R_2 = \frac{R}{6} + \frac{2R}{6} = \frac{3R}{6} = \frac{R}{2}$$

Formula for the resultant resistance for the parallel configuration:

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_3} + \frac{1}{R_{12}}$$

$$R_{\text{total}} = \frac{R_3 R_{12}}{R_3 + R_{12}} = \frac{R_3 R_{12}}{R_3 + R_{12}} = \frac{\frac{R}{2} \cdot \frac{R}{2}}{\frac{R}{2} + \frac{R}{2}} = \frac{\frac{R^2}{4}}{R} = \frac{R}{4}$$

Formula for the total current through the circuit (Ohm's law):

$$I_{\text{total}} = \frac{U}{R_{\text{total}} + r} = \frac{U}{\frac{R}{4} + r} = \frac{10V}{\frac{15 \text{ Ohm}}{4} + 1 \text{ Ohm}} = 2.1 \text{ A}$$

Resistors $R_3 = \frac{R}{2}$ and $R_{12} = \frac{R}{2}$ in a parallel configuration are each subject to the same potential difference (voltage), however the currents through them add, since $R_3 = R_{12} \Rightarrow I_3 = I_2 = \frac{I_{\text{total}}}{2} = \frac{2.105 \text{ A}}{2} = 1.05 \text{ A}$ (current is halved).

In a series configuration (resistors R_1 and R_2), the current through all of the resistors is the same:

$$I_1 = I_2 = 1.05 \text{ A}$$

Answer: $I_1 = I_2 = I_3 = 1.05 \text{ A}$;

$$I_{\text{total}} = 2.1 \text{ A}$$