

Answer on Question #44503-Physics-Electromagnetism

The length of potentiometer wire is 600cm and it carries a current of 40mA. For a cell of e.m.f. 2V and internal resistance 10ohm, the null point is found to be at 500cm. If a voltmeter is connected across the cell, the balancing length is decreased by 10cm. Find (a) the resistance of whole wire. (b) Reading of voltmeter and (c) resistance of voltmeter

Solution

$$(a) E = Kl \rightarrow K = \frac{E}{l} = \frac{2}{500} \frac{V}{cm}.$$

$$V = KL = \frac{2}{500} \cdot 600 = 2.4 V,$$

where V is the potential difference across potentiometer wire.

The resistance of potentiometer wire is

$$R = \frac{V}{I} = \frac{2.4 V}{40 \cdot 10^{-3} A} = 60 \Omega.$$

(b) On connecting voltmeter new balancing length is $l' = 490 cm$.

Reading of voltmeter is

$$U = \frac{l'}{L} V = \frac{490}{600} \cdot 2.4 = 1.96 V.$$

(c) The resistance of voltmeter is

$$R_{\text{voltmeter}} = \frac{U}{I} = \frac{1.96 V}{40 \cdot 10^{-3} A} = 49 \Omega.$$