

### Answer on Question #45669, Physics, Other

A galvanometer of resistance  $120\Omega$  a full scale deflection with a current of  $0.0005\text{A}$ . How would you convert it to an ammeter that reads a maximum current of  $5\text{A}$ ?


- a. connect  $2000\Omega$  in parallel to it
- b. connect  $200.12\Omega$  in series to it
- c. connect  $20.10\Omega$  in series to it
- d. connect  $0.012\Omega$  in parallel to it

#### Solution:

Let resistance of galvanometer  $R_g=120\Omega$  and it gives full-scale deflection when current  $I_g=0.0005\text{ A}$  is passed through it. Then,

$$V_g = I_g R_g$$

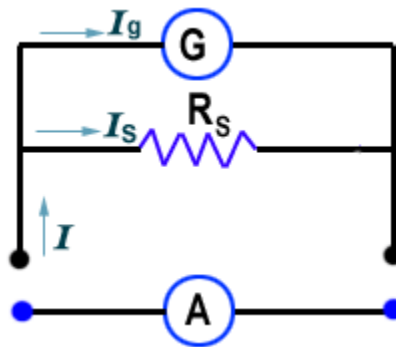Let a shunt of resistance ( $R_s$ ) is connected in parallel to galvanometer. If total current through the circuit is  $I$ .



Then current through shunt:

$$I_s = (I - I_g)$$

potential difference across the shunt:

$$V_s = I_s R_s$$

or

$$V_s = (I - I_g) R_s$$

But

$$V_s = V_g$$

$$(I - I_g) R_s = I_g R_g$$

$$R_s = \frac{I_g}{I - I_g} R_g$$

$$R_s = \frac{0.0005}{5 - 0.0005} \cdot 120 = 0.012 \Omega$$

**Answer:** d. connect  $0.012\Omega$  in parallel to it