

**Answer on Question #46804, Physics, Other**

A 9V battery is short-circuited. The potential difference across the battery is found to be 8V, and the current is 5A. What is the internal resistance of the battery?

0.1Ω

0.2Ω

0.3Ω

0.4Ω

**Solution:**

Given:

$$\varepsilon = 9 \text{ V,}$$

$$V = 8 \text{ V,}$$

$$I = 5 \text{ A,}$$

$$R_{\text{internal}} = ?$$

$$I = \frac{\varepsilon}{R + R_{\text{internal}}}$$

So,

$$\varepsilon = IR + IR_{\text{internal}}$$

$$IR = V = 8 \text{ V}$$

Thus,

$$8 = 9 - 5R_{\text{internal}}$$

$$5R_{\text{internal}} = 1$$

$$R_{\text{internal}} = 0.2 \Omega$$

**Answer:** 0.2Ω.