

Answer on Question #46854 – Physics – Solid State Physics

Two metallic wires of the same material and same length but different cross sectional areas are joined together (in series) and (in parallel) ,to a source of amf. in which of the two wires will the drift velocity of electron be more in each of the two cases and why?

Solution:

The formula for evaluating the drift velocity of electrons in a material of constant cross-sectional area is given by (A – area of cross – section of the material, I – current flowing through the material, q –the charge of the electron, n is the charge-carrier density):

$$v = \frac{I}{nAq}$$

First case: series connection

In a series circuit, the current through each of the components is the same ($I_1 = I_2$), thus drift velocity is more in wire with smaller area of cross-section:

$$\begin{aligned} v_1 &= \frac{I}{nA_1q} \\ v_2 &= \frac{I}{nA_2q} \\ A_2 > A_1 &\Rightarrow \frac{I}{nA_2q} < \frac{I}{nA_1q} \\ v_2 &< v_1 \end{aligned}$$

First case: parallel connection

In a parallel circuit, the voltage across each of the components is the same, and the total current is the sum of the currents through each component (L –length of the wire, ρ – electrical resistivity).

$$\begin{aligned} I_1 &= \frac{U}{R} = \frac{U}{\frac{\rho L}{A_1}} = \frac{UA_1}{\rho L} \\ I_2 &= \frac{U}{R} = \frac{U}{\frac{\rho L}{A_2}} = \frac{UA_2}{\rho L} \\ v_1 &= \frac{I_1}{nA_1q} = \frac{1}{nA_1q} \frac{UA_1}{\rho L} = \frac{U}{nqL} \\ v_2 &= \frac{I_2}{nA_2q} = \frac{1}{nA_2q} \frac{UA_2}{\rho L} = \frac{U}{nqL} \end{aligned}$$

According to initial condition of the task, $L_1 = L_2 = L$, $\rho_1 = \rho_2 = \rho$ (wires of the same material and same length), thus, drift velocities will be the same in both wires.

$$v_1 = v_2 = \frac{U}{nqL}$$