

## Answer on Question #47998, Physics, Electric Circuits

### Question:

In investigating an existing design of a circuit, it was found that a  $25\Omega$  resistor dissipates 9W. The engineer decides to put a  $12.5\Omega$  resistor in series with this  $25\Omega$  resistor. What is the power dissipation now in the  $25\Omega$  resistor with the same supply voltage after the  $12.5\Omega$  resistor was added? (Clue - determine what the supply voltage is from the given information. Then you can either use the voltage divider theory to find the voltage now dropped across the  $25\Omega$  and then work out the power, or you can calculate the total current now drawn by both resistors and then work out the power across the  $25\Omega$  resistor!)

### Solution:

First of all we find the supply voltage from the given information. For this purpose we write the formula for power dissipation on resistor  $R_1$ :

$$P = U_{\text{supply}} \times I_1,$$

where  $P$  is the power dissipation on resistor  $R_1$ ,  $U_{\text{supply}}$  is the supply voltage,  $I_1$  is the current that flows through the resistor  $R_1$ .

Used the Ohm's law we expressed  $I_1$  in terms of  $R_1$  and  $U_{\text{supply}}$ :

$$I_1 = \frac{U_{\text{supply}}}{R_1}.$$

Substituting  $I_1$  in the expression for power dissipation on resistor  $R_1$  we obtain:

$$P = \frac{(U_{\text{supply}})^2}{R_1},$$

$$U_{\text{supply}} = \sqrt{P \times R_1} = \sqrt{9W \times 25\Omega} = 15V.$$

From the voltage divider theory we can find voltage drops across the resistor  $R_1$ :

$$U_1 = U_{\text{supply}} \times \frac{R_1}{(R_1 + R_2)} = \frac{15V \times 25\Omega}{(25\Omega + 12.5\Omega)} = \frac{375V \times \Omega}{37.5\Omega} = 10V.$$

Then we can find the current  $I_1$  after the resistor  $R_2$  was added:

$$I_1 = \frac{U_1}{R_1} = \frac{10V}{25\Omega} = 0.4A$$

Finally we can obtain the power dissipation on resistor  $R_1$  after the resistor  $R_2$  was added:

$$P = U_1 \times I_1 = 10V \times 0.4A = 4W$$

**Answer:**

$$P = 4W$$