

**Answer on Question #48187, Physics, Electric Circuits** A capacitor of value 10 micro Farads is connected in series with a resistor of value 10 ohms. Calculate the value of the time constant.

Solution

Time constant is

$$\tau = R \cdot C = 10\Omega \cdot 10^{-6} F = 10^{-4} s$$