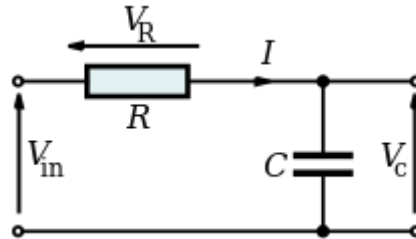


### Answer on Question #50347, Physics, Electric Circuits

Calculate the ratio  $V_C/V$  at the turn-over frequency (sometimes called the break frequency) if  $R=1\text{k}\Omega$  and  $C=2\mu\text{F}$ .

**Solution:**



By viewing the circuit as a voltage divider, the voltage across the capacitor is:

$$V_C = \frac{1}{1 + sRC} V$$

where  $s = j\omega$ .

Generally we will be interested only in the magnitude of the response:

$$\left| \frac{V_C}{V} \right| = \left| \frac{1}{1 + sRC} \right| = \frac{1}{\sqrt{1^2 + (\omega RC)^2}}$$

At  $\omega=1/RC$ , called the break frequency (or cutoff frequency, or 3dB frequency, or half-power frequency, or bandwidth), the magnitude of the gain is

$$\left| \frac{V_C}{V} \right| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}}$$

**Answer:**  $\left| \frac{V_C}{V} \right| = \frac{1}{\sqrt{2}}$