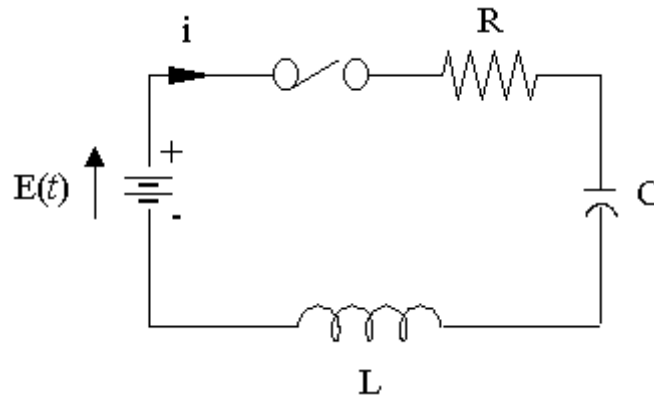


Answer on Question #50741, Physics, Other

A series circuit consists of a resistor with $R = 20\text{ohm}$, an inductor with $L = 1\text{H}$, a capacitor with $C = 0.002\text{ F}$, and a 12 V battery. IF the initial charge and current are both 0, find the charge and current at time t .

Solution:



Consider a series RLC circuit (one that has a resistor, an inductor and a capacitor) with a constant driving electro-motive force (emf) E . The current equation for the circuit is

$$L \frac{di}{dt} + Ri + \frac{Q}{C} = E$$

Since , this equation becomes

$$L \frac{d^2Q}{dt^2} + \frac{RdQ}{dt} + \frac{Q}{C} = E$$

With the given values of R , L , C and E , the last equation becomes

$$\frac{d^2Q}{dt^2} + 20 \frac{dQ}{dt} + \frac{Q}{0.002} = 12$$

$$\frac{d^2Q}{dt^2} + 20 \frac{dQ}{dt} + 500Q = 12$$

The auxiliary equation is

$$r^2 + 20r + 500 = 0$$

with roots

$$r = -10 - 20i$$

$$r = -10 + 20i$$

so the solution of the complementary equation is

$$Q_c(t) = e^{-10t}(c_1 \cos 20t + c_2 \sin 20t)$$

For the method of undetermined coefficients we try the particular solution

$$Q_p(t) = A$$

$$500A = 12$$

$$\text{or } A = \frac{3}{125} = 0.024$$

The general solution is

$$Q(t) = Q_c(t) + Q_p(t) = e^{-10t}(c_1 \cos 20t + c_2 \sin 20t) + 0.024$$

But

$$Q(0) = 0 = c_1 + 0.024$$

$$c_1 = -0.024$$

The current

$$I(t) = Q'(t) = e^{-10t}[(-10c_1 + 20c_2) \cos 20t + (-10c_2 - 20c_1) \sin 20t]$$

$$I(0) = 0 = -10c_1 + 20c_2$$

Thus

$$c_2 = \frac{c_1}{2} = -0.012$$

Hence the charge is

$$\begin{aligned} Q(t) &= e^{-10t}(-0.024 \cos 20t - 0.012 \sin 20t) + 0.024 = \\ &= -0.012e^{-10t}(2 \cos 20t + \sin 20t) + 0.024 \end{aligned}$$

The current is

$$\begin{aligned} I(t) = Q'(t) &= e^{-10t}[(10 * 0.024 - 20 * 0.012) \cos 20t + (10 * 0.012 + 20 * 0.024) \sin 20t] = \\ &= e^{-10t}(0.6) \sin 20t \end{aligned}$$

Answer: $Q(t) = -0.012e^{-10t}(2 \cos 20t + \sin 20t) + 0.024$

$$I(t) = 0.6e^{-10t} \sin 20t$$

<http://www.AssignmentExpert.com/>