

Answer on Question #51520, Physics, Electromagnetism

an ac circuit consist of a voltage source $v = 200\sin 120\pi t$ and a 6uf capacitor in series. calculate the current established in the circuit

- a) 0.32A
- b) 1.24A
- c) 0.64A
- d) 2.13A

Solution

We represent the voltage in complex form

$$\dot{U} = \frac{120}{\sqrt{2}} \text{ V} \quad (1)$$

The resistance of the capacitor is given by Eq.(2)

$$Z = -jX_c = -j \frac{1}{\omega C} = -j \frac{1}{120\pi \cdot 6 \cdot 10^{-6}} \approx -442j \text{ Om} \quad (2)$$

The current established in the circuit is given by Eq.(3)

$$I = \left| \frac{\dot{U}}{Z} \right| = \left| \frac{200/\sqrt{2}}{-442j} \right| \approx 0.32A \quad (3)$$

Answer: a) 0.32A