

Answer on question #51578, Physics / Electric Circuits

Question An electrical source with internal resistance r is used to operate a lamp of resistance R . What fraction of the total power is delivered to the lamp?

Solution We suppose that internal and external resistance are connected in series. Hence, they have same current. Power is

$$P = I^2 R$$

Hence, fractions of energy are proportional to resistance. To lamp is delivered

$$\frac{R}{R + r}$$