

### Answer on Question#53161 - Physics - Electric Circuits

A potentiometer wire has length  $l = 4$  m and resistance  $R = 8$  ohm. The resistance  $r$  that must be connected in series with the wire and an accumulator of e.m.f  $\varepsilon = 2$  V, so as to get a potential gradient  $F = 1$  mV per cm on the wire is- A) 44 ohm B) 48 ohm C) 32 ohm D) 40 ohm

Solution:

The potential drop through the potentiometer should be

$$V_R = F \cdot l$$

Since the potentiometer is connected in series with resistance  $r$ , this potential drop can also be expressed through the e.m.f:

$$V_R = \frac{R}{R + r} \varepsilon$$

Therefore we obtain an equation for  $r$ :

$$\frac{R}{R + r} \varepsilon = F \cdot l$$
$$r = \frac{R(\varepsilon - F \cdot l)}{F \cdot l} = \frac{8\Omega \left( 2V - 1 \frac{\text{mV}}{\text{cm}} \cdot 4\text{m} \right)}{1 \frac{\text{mV}}{\text{cm}} \cdot 4\text{m}} = 39992 \Omega$$

Answer: 39992  $\Omega$ .