Answer on Question# 55416 - Physics - Electric Circuits

supplied during rectification is

Rectifier	
Filter	
Choke	
Schmitt Trigger	
Solution.	
Filter	
Answer:	
Filter	

http://www.AssignmentExpert.com/

The circuit responsible for the removal of flunctuation or pulsation present in the output voltage