

### **Answer on Question#55417 — Physics — Electric circuits**

The \_\_\_\_\_ is the preferred choice in the design of amplifiers.

Common Base

Common Collector

Common Emitter

Shunt

**Answer:** Common Emitter

<http://www.AssignmentExpert.com/>