

Answer on Question#55418— Physics — Electric circuits

The major difference between the bridge rectifier and centre tap rectifier is that the bridge requires 4 diodes while the full wave centre tapped rectifier requires a centre tapped _____.

Repeater

Transistor

Transformer

Amplifier

Answer: Transformer

<http://www.AssignmentExpert.com/>