

### **Answer on Question#55421— Physics — Electric circuits**

In negative feedback, the feedback voltage is \_\_\_\_\_ degrees out of phase with the input voltage.

270

180

45

90

**Answer: 180**

<http://www.AssignmentExpert.com/>