

Answer on Question#55422— Physics — Electric circuits

The transistor will operate as a switch when it is biased in the

Saturation Region

Cut-off region

Forward Region

Reverse Region

Answer: either saturation or cut-off region