

Answer on Question #55427, Physics Electric Circuits

In _____ , the transistor operates somewhere between saturation and cut-off state.

Step-down Regulator

Step-up Regulator

Linear Regulator

Inverting Regulator

Answer: Linear Regulator