

Answer on Question #55430, Physics Electric Circuits

A major disadvantage of the _____ pass transistor regulator is that they are inefficient

parallel

linear

series,

one.

Answer: linear

Linear regulators are often inefficient: since the transistor is acting like a resistor, it will waste electrical energy by converting it to heat.