

Answer on Question#55887 - Physics - Electromagnetism

A galvanometer with coil resistance $r = 12.0\Omega$ shows full scale deflection for a current of $I_g = 2.5\text{mA}$. How would you convert it into a voltmeter of range $V_{min} = 0$ to $V_{max} = 10.0\text{V}$?


3988 Ω in series

0.43 Ω in parallel

2000 Ω in parallel

1.62 Ω in series

Solution:

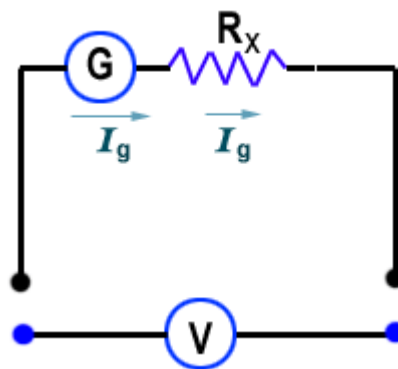

To convert galvanometer into a voltmeter we should add some resistance R_x in series. To find this resistance we must take into account that the sum of voltage drops in r and R_x for I_g equals V_{max} :

$$I_g(r + R_x) = V_{max}$$

Therefore

$$R_x = \frac{V_{max}}{I_g} - r = \frac{10\text{V}}{2.5\text{mA}} - 12\Omega = 3988\Omega$$

Answer: 3988 Ω in series.