

Answer on Question#55890 - Physics - Electromagnetism

An air-cored transformer is assumed to be 100% efficient. The ratio of the secondary turns N_S to the primary turns N_P is 1:20. A $V_P = 240\text{V}$ ac supply is connected to the primary coil and a $R = 6\Omega$ load is connected to the secondary coil. What is the current in the primary coil?

0.10A

0.14A

2.0A

40.0A

Solution:

According to the ideal transformer identity

$$\frac{V_S}{V_P} = \frac{I_P}{I_S} = \frac{N_S}{N_P}$$

Therefore

$$V_S = \frac{N_S}{N_P} V_P = \frac{1}{20} 240\text{V} = 12\text{V}$$

The current in the secondary coil is

$$I_S = \frac{V_S}{R} = \frac{12\text{V}}{6\Omega} = 2\text{A}$$

The current in the primary coil

$$I_P = \frac{N_S}{N_P} I_S = \frac{1}{20} 2\text{A} = 0.1\text{A}$$

Answer: 0.10A.