

Answer on Question #56003, Physics / Other

Task: The maximum possible efficiency of the half wave rectifier is _____.

- a) 40.60%
- b) 50.6%
- c) 70%
- d) 30%

Answer: a) 40.60%

Rectification efficiency is defined as the ratio between the output power to the ac input power.

Efficiency, $\eta = \text{DC power delivered to the load} / \text{AC input power from the transformer} = P_{dc} / P_{ac}$

DC power delivered to the load, $P_{dc} = I_{dc}^2 R_L = (I_{max}/\pi)^2 R_L$

AC power input to the transformer, $P_{ac} = \text{Power dissipated in diode junction} + \text{Power dissipated in load resistance } R_L$

$= I_{rms}^2 R_F + I_{rms}^2 R_L = \{I_{MAX}^2/4\} [R_F + R_L]$

So, Rectification Efficiency, $\eta = P_{dc} / P_{ac} = \{4/\pi^2\} [R_L / (R_F + R_L)] = 0.406 / \{1 + R_F/R_L\}$

The maximum efficiency that can be obtained by the half wave rectifier is 40.6%. This is obtained if R_F is neglected.