


## Answer on Question 58886, Physics, Electric Circuits

### Question:

A 3 V battery with internal resistance  $0.5 \Omega$  is connected across a parallel combination of  $1 \Omega$  and  $2 \Omega$  resistances. The current in the  $2 \Omega$  resistance is \_\_\_\_?

### Solution:

Here's the sketch of our task:

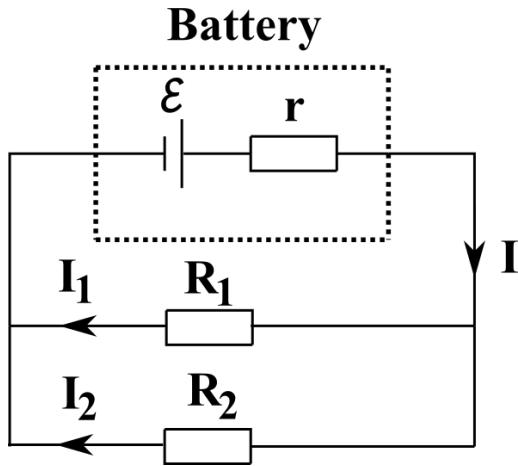

We have a battery with electromotive force of  $\mathcal{E} = 3 \text{ V}$ ; the internal resistance of the battery is  $r = 0.5 \Omega$ . That battery is connected across a parallel combination of  $R_1 = 1 \Omega$  and  $R_2 = 2 \Omega$  resistances, as shown in the picture above. Our task is to find the current in the resistance  $R_2$ .

Let's first find the equivalent resistance of combination of resistances  $R_1 = 1 \Omega$  and  $R_2 = 2 \Omega$  that connected in parallel (let's call it the equivalent load resistance):

$$R_{eq(load)} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2} = \frac{1 \Omega \cdot 2 \Omega}{1 \Omega + 2 \Omega} = 0.66(6) \Omega.$$

The combination of these two resistances is in series with the internal resistance of the battery,  $r$ . Let's find the equivalent resistance of the internal resistance of the battery,  $r$ , and the equivalent load resistance,  $R_{eq(load)}$ :

$$R_{eq} = r + R_{eq(load)}.$$

Then, from the Ohm's law we can find the current in the circuit:

$$I = \frac{\mathcal{E}}{R_{eq}} = \frac{\mathcal{E}}{r + R_{eq(load)}} = \frac{3 \text{ V}}{0.5 \Omega + 0.66(6) \Omega} = 2.57 \text{ A.}$$

So, the terminal voltage of the battery will be:

$$V = \mathcal{E} - Ir = 3 \text{ V} - 2.57 \text{ A} \cdot 0.5 \Omega = 1.715 \text{ V.}$$

Finally, from the Ohm's law we can find the current in the  $R_2 = 2 \Omega$  resistance:

$$I_2 = \frac{V}{R_2} = \frac{1.715 \text{ V}}{2 \Omega} = 0.86 \text{ A.}$$

**Answer:**

$$I_2 = 0.86 \text{ A.}$$