


## Answer on Question 59058, Physics, Electric Circuits

### Question:

A  $2\ \Omega$  and a  $3\ \Omega$  resistors in parallel are connected in series to a  $4\ \Omega$  resistor. The combination is then connected across a  $12\ V$  battery having internal resistance of  $1\ \Omega$ . What is the equivalent resistance of the circuit?

### Solution:

Here's the sketch of our task:

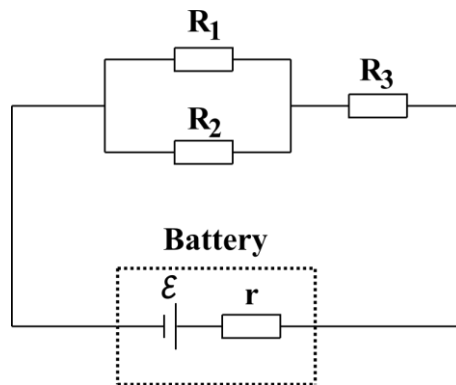

We have a parallel combination of  $R_1 = 2\ \Omega$  and  $R_2 = 3\ \Omega$  resistors that are connected in series to a  $R_3 = 4\ \Omega$  resistor. The combination is then connected across a  $12\ V$  battery having internal resistance of  $r = 1\ \Omega$ . Our task is to find the equivalent resistance of the circuit.

Let's first find the equivalent resistance of combination of resistors  $R_1 = 2\ \Omega$  and  $R_2 = 3\ \Omega$  that connected in parallel:

$$R_{12(\parallel)} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2} = \frac{2\ \Omega \cdot 3\ \Omega}{2\ \Omega + 3\ \Omega} = 1.2\ \Omega.$$

Then, from our sketch we can see that  $R_{12(\parallel)}$ ,  $R_3$  and  $r$  are connected in series. Therefore, the equivalent resistance of the circuit will be:

$$R_{eq} = R_{12(\parallel)} + R_3 + r = 1.2\ \Omega + 4\ \Omega + 1\ \Omega = 6.2\ \Omega.$$

**Answer:**  $R_{eq} = 6.2\ \Omega$ .