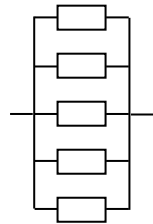



Answer on Question #60612 – Physics – Electric Circuits

What is the minimum resistance which can be made by using five resistors of 25ohms each


**Solution.** It is obvious that the parallel connection of conductors has a smaller series resistance. Consider the different connections of conductors and find the final resistance  
Consider the different connections of conductors and find the final resistance



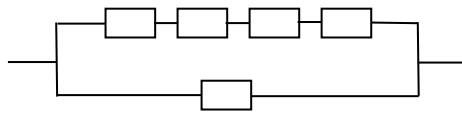
$$\frac{1}{R'} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \frac{1}{R} \rightarrow R' = 5 \text{ ohms}$$



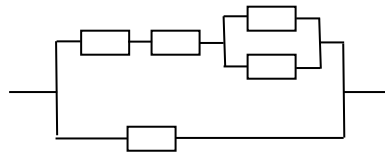
$$\frac{1}{R'} = \frac{1}{R} + \frac{1}{4R} \rightarrow R' = \frac{4}{5}R = 20 \text{ ohms}$$



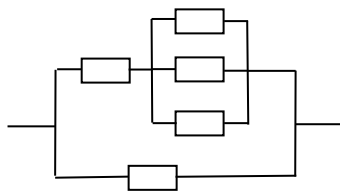
$$\frac{1}{R'} = \frac{1}{\frac{5}{2}R} + \frac{1}{R} \rightarrow R' = \frac{5}{7}R = \frac{125}{7} \text{ ohms}$$



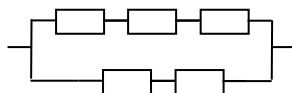
$$\frac{1}{R'} = \frac{1}{\frac{4}{3}R} + \frac{1}{R} \rightarrow R' = \frac{4}{7}R = \frac{100}{7} \text{ ohms}$$



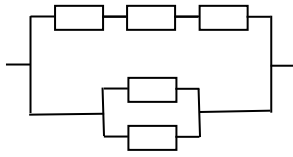
$$\frac{1}{R'} = \frac{1}{3R} + \frac{1}{2R} \rightarrow R' = \frac{6}{5}R = 30 \text{ ohms}$$



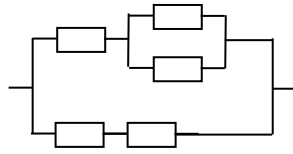
$$\frac{1}{R'} = \frac{1}{3R} + \frac{1}{\frac{1}{2}R} \rightarrow R' = \frac{3}{7}R = \frac{75}{7} \text{ ohms}$$


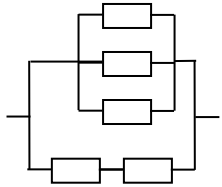
$$\frac{1}{R'} = \frac{1}{2R} + \frac{1}{\frac{3}{2}R} \rightarrow R' = \frac{6}{7}R = \frac{150}{7} \text{ ohms}$$


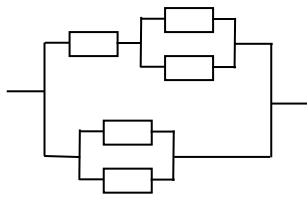
$$\frac{1}{R'} = \frac{1}{2R} + \frac{1}{\frac{1}{3}R} \rightarrow R' = \frac{2}{7}R = \frac{50}{7} \text{ ohms}$$



$$\frac{1}{R'} = \frac{1}{\frac{1}{2}R} + \frac{1}{\frac{3}{2}R} \rightarrow R' = \frac{3}{8}R = \frac{75}{8} \text{ ohms}$$

Hence the minimum resistance which can be made by using five resistors of 25ohms each equal 5 ohms.

**Answer:** Minimum resistance 5ohms.