

**Answer on question #61351, Physics, Electromagnetism**

**7)** A capacitor of  $2.0\mu F$  is connected to a battery of  $2.0V$  through a resistance of  $10k\Omega$ . What is the initial current in the circuit and the current after  $0.02s$ ?

- a)  $0.5\mu A$  and  $0.074mA$
- b)  $7.4A$  and  $5.0mA$
- c)  $0.2\mu A$  and  $0.074mA$
- d)  $6.2\mu A$  and  $7.04mA$

**Solution:**

Current across the capacitor equals:

$$I = \frac{V}{R} \cdot e^{-\frac{t}{RC}}$$

When  $t = 0 s$

$$I = \frac{2.0 V}{10 \cdot 10^3 \Omega} \cdot e^{-\frac{0.0s}{10 \cdot 10^3 \Omega \times 2.0 \cdot 10^{-6} F}} = 0.2 mA$$

When  $t = 0.02 s$

$$I = \frac{2.0 V}{10 \cdot 10^3 \Omega} \cdot e^{-\frac{0.02s}{10 \cdot 10^3 \Omega \times 2.0 \cdot 10^{-6} F}} = 0.074 \cdot 10^{-3} A = 0.074 mA$$

**Answer:** 0.2 mA and 0.074 mA

**8)** A conductor  $2cm$  long carrying a current of  $8A$  lies at right angles to a magnetic field of which the flux density is  $1.0T$ . Calculate the force exerted on the conductor?

- a)  $0.20N$
- b)  $0.16N$
- c)  $0.25N$
- d)  $0.45N$

**Solution:**

Ampere force module can be found with the formula:

$$F = IBl \cdot \sin\alpha$$

where  $\alpha$  is the angle between magnetic induction and the direction along which the current flows (we know that  $\alpha = 90^\circ$ ).

$$F = 8 A \cdot 1.0T \cdot 0.02 m \cdot \sin 90^\circ = 0.16 N$$

**Answer:** 0.16 N