

## Answer on Question#61363 – Physics – Electromagnetism

11) An air-cored transformer is assumed to be 100% efficient. The ratio of the secondary turns to the primary turns is 1:20. A 240V ac supply is connected to the primary coil and a 6Ω load is connected to the secondary coil. what is the current in the primary coil?

- a) 0.10A
- b) 0.14A
- c) 2.0A
- d) 40.0A

**Solution.** According to the conditions of the problem  $\frac{N_2}{N_1} = \frac{1}{20}$ ,  $R_2 = 6\Omega$  where  $N_1, N_2$  – turns in primary and secondary coil,  $R_2$  – resistor secondary coil. Using formula for transformer  $\frac{V_2}{V_1} = \frac{N_2}{N_1}$  ( $V_1, V_2$  – voltage in primary and secondary coil.). Therefore  $V_2 = V_1 \frac{N_2}{N_1} \rightarrow V_2 = 240 \frac{1}{20} = 12V$ .

Using Ohm's law  $I = \frac{V}{R}$  find current in secondary coil.  $I_2 = \frac{12}{6} = 2A$ .

From definition electric power  $P = VI$ . For secondary coil power  $P_2 = 12 \cdot 2 = 24W$ .

An air-cored transformer is assumed to be 100% efficient. Hence  $P_1 = P_2$ .

$$V_1 I_1 = V_2 I_2 \rightarrow I_1 = \frac{V_2 I_2}{V_1} = \frac{24}{240} = 0.1A$$

**Answer.** a) 0.1A.

12) A voltmeter connected across a 60Hz ac source reads 240V. Write down the expression of the instantaneous voltage as a function of time.

- a)  $240\sin 339.4t$
- b)  $339.4\sin 377t$
- c)  $377\cos 339.4t$
- d)  $240\cos 339.4t$

**Solution.** The General equation of the instantaneous voltage of the alternating current has the form  $V = V_0 \sin \omega t = V_0 \sin 2\pi f t$ , where  $V_0$  – peak voltage,  $f$  – frequency. Using relationship between peak voltage and rms voltage  $V = \frac{V_0}{\sqrt{2}}$ . A voltmeter show rms voltage hence peak voltage  $V_0 = V\sqrt{2} = 240\sqrt{2} \approx 339.4V$ .

$$2\pi f = 2\pi \cdot 60 \approx 377 \frac{rad}{s}$$
 Therefore

$$V = 339.4 \sin 377t$$

**Answer.** b)  $339.4 \sin 377t$ .