

Answer Question#61364 Physics – Electromagnetism

13) An ac circuit consists of voltage source $V = 200 \sin 120\pi t$ and a $6\mu F$ capacitor in series. Calculate the current establish in the circuit

- a) 0.32A
- b) 1.24A
- c) 0.64A
- d) 2.13A

Solution. Capacitive reactance can be calculate using formula $X_C = \frac{1}{\omega C}$ (where $\omega = 2\pi f$, f – frequency, C – capacitance). Using Ohm's law $I = \frac{V}{X_C}$. Hence $I = \frac{V}{X_C} = \frac{200 \sin 120\pi t}{\frac{1}{\omega C}} = 200\omega C \sin 120\pi t$.

$$I = 200\omega C \sin 120\pi t = 200 \cdot 120\pi \cdot 6 \cdot 10^{-6} \sin 120\pi t = 0.452 \sin 120\pi t$$

$$I_{\max} = 0.452A. \text{ The current establish in the circuit } I = \frac{I_{\max}}{\sqrt{2}} = \frac{0.452}{\sqrt{2}} \approx 0.32A.$$

Answer. a) 0.32A

14) An RLC circuit contains an as voltage source with rms value of 50V and has frequency of 600Hz. Suppose that a resistance $R = 20\Omega$, capacitance $C = 10.0\mu F$ and an inductance $L = 4.0mH$ are connected in series to the source. Find the current in the circuit and the voltmeter reading across the inductor.

- a) 2.17A and 32.8V
- b) 1.6A and 24.2V
- c) 0.13A and 12.1V
- d) 4.0A and 23.1V

Solution. We can find capacitive reactance and inductive reactance using formula:

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}, X_L = \omega L = 2\pi f L.$$

According to the condition of the problem $f = 600Hz$ – frequency; $L = 4 \cdot 10^{-3}H$ – inductance, $C = 10.0 \cdot 10^{-6}F$ – capacitance. Substituting these values get

$$X_C = \frac{1}{2\pi \cdot 600 \cdot 10.0 \cdot 10^{-6}} \approx 26.5\Omega$$

$$X_L = 2\pi \cdot 600 \cdot 4 \cdot 10^{-3} \approx 15.1\Omega$$

We can find impedance of an RLC series circuit using formula:

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \rightarrow Z = \sqrt{20^2 + (15.1 - 26.5)^2} \approx 23\Omega.$$

$$\text{Find current using Ohm's law formula: } I = \frac{V}{Z} \rightarrow I = \frac{50V}{23\Omega} \approx 2.17A.$$

Using Ohm's law formula for inductor get $I = \frac{V_L}{X_L} \rightarrow V_L = IX_L = 2.17 \cdot 15.1 \approx 32.8V$. (current same because in series).

Answer. a) 2.17A and 32.8V.