

### Answer on question #61367, Physics / Electromagnetism

19) The half-life of a certain radioactive isotope is 32 hours. What fraction of the sample would remain after 16 hours?

- a) 0.50
- b) 0.25
- c) 0.62
- d) 0.71

**Solution:**

The law of radioactive decay is

$$N = N_0 \cdot 2^{-\frac{t}{T}}$$

Here  $N$  is the quantity at time  $t$ , and  $N_0$  is the initial quantity, i.e. the quantity at time  $t = 0$ ,  $T$  is the half-life.

From here,

$$\frac{N}{N_0} = 2^{-\frac{t}{T}}$$
$$\frac{N}{N_0} = 2^{-\frac{16}{32}} = 2^{-\frac{1}{2}} = 0.71$$

**Answer:** d) 0.71

20) A potentiometer wire of length 100 cm has a resistance of  $10\Omega$ . It is connected in series to a resistance  $R$  and a cell of emf 2V and negligible internal resistance. A source of emf of 10mV is balanced by a length of 40cm of the potentiometer wire. What is the value of the resistance  $R$ ?

- a)  $200\Omega$
- b)  $950\Omega$
- c)  $2000\Omega$
- d)  $790\Omega$

**Solution:**

The current in the circuit

$$I = \frac{U}{R + r}$$

Now as the 100 cm wire has a resistance of  $10\Omega$ , the resistance of 40 cm of wire will be  $40 \times (10/100) = 4\Omega$ .

Potential drop across 40 cm wire will be

$$V = 4I$$

$$I = \frac{2}{R + 10}$$

given  $V = 10 \text{ mv}$

$$10 \cdot 10^{-3} = 4 \cdot \frac{2}{R + 10}$$

$$R = 4 \cdot \frac{2}{10 \cdot 10^{-3}} - 10$$

$$R = 790 \Omega$$

**Answer:** d) 790  $\Omega$

<https://www.AssignmentExpert.com>