

Answer on Question#63147 – Physics – Electric Circuits

When a battery is connected to a $103.0\text{-}\Omega$ resistor, the current is 3.05 A . When the same battery is connected to a $400.0\text{-}\Omega$ resistor, the current is 0.798 A . Find the internal resistance of the battery.

Solution. Using relationship for electromotive force and internal resistance

$$\varepsilon = I(R + r)$$

ε – electromotive force in volts;

I – current in amperes;

R – resistance of the load in the circuit in ohms;

r – internal resistance of the battery in ohms.

For battery ε , r – constant value.

Write a system of equations for different resistances of the load

$$\begin{cases} \varepsilon = I_1(R_1 + r) \\ \varepsilon = I_2(R_2 + r) \end{cases}$$

According to the condition of the problem

$$I_1 = 3.05\text{ A} \quad R_1 = 103\Omega$$

$$I_2 = 0.798\text{ A} \quad R_2 = 400\Omega$$

$$\text{Hence } I_1(R_1 + r) = I_2(R_2 + r) \quad r = \frac{I_2R_2 - I_1R_1}{I_1 - I_2} = \frac{0.798 \cdot 400 - 3.05 \cdot 103}{3.05 - 0.798} \approx 2.24\Omega.$$

Answer. 2.24Ω

<https://www.AssignmentExpert.com>