

## Answer on Question 65664, Physics, Electric Circuits

### Question:

A  $2.0\ \Omega$ , a  $13.0\ \Omega$  and  $16.0\ \Omega$  resistor are connected in series with a  $24.0\ V$  battery. Calculate the equivalent resistance.

### Solution:

We can find the equivalent resistance of a series combination of three resistors from the formula:

$$R_{eq} = R_1 + R_2 + R_3 = 2.0\ \Omega + 13.0\ \Omega + 16.0\ \Omega = 31\ \Omega.$$

### Answer:

$$R_{eq} = 31\ \Omega.$$

Answer provided by <https://www.AssignmentExpert.com>