

A 11- coffee maker and a 15- frying pan are connected in series across a 120-V source of voltage. A 24- bread maker is also connected across the 120-V source and is in parallel with the series combination. Find the total current supplied by the source of voltage.

Answer

$$R_1(\text{resistance of coffee maker}) = 11 \text{ Ohm}, R_2(\text{resistance of frying pan}) \\ = 15 \text{ Ohm}, R_3(\text{resistance of bread maker}) = 24 \text{ Ohm}$$

For serial connection:

$$R_{12} = R_1 + R_2 = 26 \text{ Ohm}$$

For parallel connection:

$$R = \frac{R_{12}R_3}{R_{12} + R_3} = 12,48 \text{ Ohm}$$

The total current supplied by the source of voltage

$$I = \frac{U}{R} = \frac{120\text{V}}{12,48 \text{ Ohm}} = 9,61538 \text{ A}$$