

## Answer on Question #66331 - Physics - Electric Circuits

### Question

A 100-volt electromotive force is applied to an R-C series circuit in which the resistance R is 200 ohms and the capacitance C is  $10^{-4}$  farad. find the charge  $q(t)$  on the capacitor if  $q(0) = 0$ .

### Solution

*The charge on the plates of the capacitor:*

$$Q = C \times V_c$$

*For RC charging circuit voltage across the capacitor is:*

$$V_c(t) = V_s \times (1 - e^{-t/RC}) = 100 \times (1 - e^{-t/200 \times 10^{-4}}) = 100 \times (1 - e^{-\frac{t}{0.02}}) = 100 \times (1 - e^{-t \times 50})$$

$V_c$  - is the voltage across the capacitor

$V_s = 100$  - is the supply voltage

$t$  - elapsed time since the application of the supply voltage

$RC$  - time constant of the RC charging circuit

*Charge*

$$q(t) = C \times V_c(t) = 10^{-4} \times 100 \times (1 - e^{-\frac{t}{0.02}})$$

### Answer

$$q(t) = C \times V_c(t) = 10^{-4} \times 100 \times (1 - e^{-50t})$$